

## Electrician - Block 1 - Module 2 : Basic Electrical - AC circuits

### Questions: Level 1


1 How many electrons are there in the copper atom?

- A 8
- B 13
- C 18
- D 29

2 What is the formula to calculate the equivalent resistance ( $R_T$ ) of the three resistors  $R_1$ ,  $R_2$  &  $R_3$  are connected in parallel circuit?

- A  $R_T = R_1 + R_2 + R_3$
- B  $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
- C  $R_T = \frac{1}{R_1 + R_2 + R_3}$
- D  $R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

3 What is the name of the resistor?

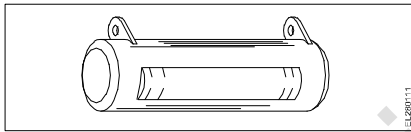

- A Metal film resistor
- B Wire wound resistor
- C Carbon – film resistor
- D Carbon composition resistor

4 What electrical quantities are related in Ohm's law?

- A Current, resistance and power
- B Current, voltage and resistivity
- C Current, voltage and resistance
- D Voltage, resistance and current density

5 What is the unit of resistivity?

- A ohm / cm
- B ohm / cm<sup>2</sup>
- C ohm - metre
- D ohm / metre

6 What is the formula for Quantity of electricity (Q)?

- A Current x Time
- B Voltage x Current
- C Current x Resistance
- D Voltage x Resistance

7 What is the unit of conductance??

- A Mho
- B Ohm
- C Ohm-m
- D Ohm/m

8 What is the S.I unit of specific resistance?

- A Ohm/cm
- B Ohm/metre<sub>2</sub>
- C Ohm-metre
- D Micro ohm/cm<sub>2</sub>

9 Which formula is used to calculate the power of a DC circuit?

- A Voltage x time
- B Current x voltage
- C Current x resistance
- D Voltage x resistance

10 What is the specific resistance value of copper conductor?

- A 1.72 Ohm/cm<sup>3</sup>
- B 1.72 Micro ohm
- C 1.72 Micro ohm/cm<sup>3</sup>
- D 1.72 Micro ohm/m

11 What is the formula to find 3 phase Reactive power (Pr) if the line voltage is ' $V_L$ ' and line current is ' $I_L$ '?

- A  $P_r = V_L I_L$
- B  $P_r = 3 V_L I_L \cos \theta$
- C  $P_r = \sqrt{3} V_L I_L \sin \theta$
- D  $P_r = \sqrt{3} V_L I_L \cos \theta$

12 What is the formula for Reactive Power (Pr) in an AC circuit?

- A  $P_r = VI$
- B  $P_r = \sqrt{2}VI$
- C  $P_r = VI \cos \theta$
- D  $P_r = VI \sin \theta$

13 What is the phase displacement in a 3-phase AC circuit?

- A 90°
- B 120°
- C 180°
- D 270°

---

**14** What is the formula to calculate the impedance (Z) of the R.L.C series circuit, if the inductive reactance ( $X_L$ ) is less than capacitive reactance ( $X_C$ )?

**A**  $Z = R^2 + \sqrt{X_L^2 + X_C^2}$

**B**  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

**C**  $Z = \sqrt{R^2 + (X_L^2 - X_C)^2}$

**D**  $Z = \sqrt{R^2 + (X_C - X_L)^2}$

---

**15** What is the formula to calculate the three phase active power (P) if the line voltage ( $V_L$ ) and line current is  $I_L$  and phase angle is 'q'?

**A**  $P = 3 V_L I_L \sin\theta$

**B**  $P = 3 V_L I_L \cos\theta$

**C**  $P = \sqrt{3} V_L I_L \sin\theta$

**D**  $P = \sqrt{3} V_L I_L \cos\theta$

---

**16** What is the form factor ( $K_f$ ) for sinusoidal AC?

**A** 1

**B** 1.11

**C** 2.22

**D** 4.44

---

**17** Which formula is used to calculate the impedance (z) of a RLC series circuit?

**A**  $Z = R^2 + (X_L \sim X_C)^2$

**B**  $Z = \sqrt{R^2 + (X_L \sim X_C)}$

**C**  $Z = \sqrt{R + (X_L \sim X_C)}$

**D**  $Z = \sqrt{R^2 + (X_L \sim X_C)^2}$

---

**18** How many electrons are there in the valence shell of a copper atom?

**A** 1

**B** 2

**C** 8

**D** 18

---

**19** What is the unit for Quantity of electricity?

**A** Mho

**B** Coulomb

**C** Volt /second

**D** Ampere/second

---

**20** What formula is used to calculate Electro Motive Force (EMF)??

**A** EMF = Potential difference – voltage drop

**B** EMF = Potential difference + voltage drop

**C** EMF = Potential difference + voltage drop/2


**D** EMF = Potential difference + 2 x voltage drop

---

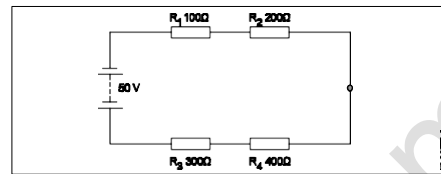**Questions: Level 2**


- 1 Calculate the electrical energy in unit consumed by 500W lamp for 5 hours.
- A 0.5 unit  
B 1.0 unit  
C 1.5 unit  
D 2.5 unit
- 2 What is the value of hot resistance of a bulb rated as 100W/250V?
- A 31.25 ohm  
B 62.50 ohm  
C 312.50 ohm  
D 625.00 ohm
- 3 Calculate the total power of the circuit of two lamps rated as 200W/240V are connected in series across 240V supply?
- A 50 W  
B 100 W  
C 200 W  
D 400 W
- 4 What is the change of resistance value of the conductor as its diameter is doubled?
- A Increases to two times  
B Decreases to four times  
C Decrease to half of the value  
D No change in value of resistance
- 5 What is the effect of the parallel circuit with one branch opened?
- A Current will remain same  
B Whole circuit will not function  
C No current will flow in that branch  
D Voltage drop increase in the opened branch
- 6 Which is the application of series circuit?
- A Voltmeter connection  
B Lighting circuits in home  
C Shunt resistor in ammeter  
D Multiplier resistor of a voltmeter
- 7 What is the effect on opened resistor in series circuit?
- A No effect in opened resistor  
B Full circuit current will flow in opened resistor  
C Total supply voltage will appear across the opened resistor  
D No voltage will appear across the opened resistor

- 8 Which type of meter is used to test the polarity of battery?
- A Moving iron ammeter  
B Moving coil voltmeter  
C Moving iron voltmeter  
D Dynamo meter type wattmeter
- 9 What is the voltage drop in resistor ' $R_2$ ' in the series circuit?



- A 5 volt  
B 10 volt  
C 15 volt  
D 20 volt
- 10 Which is the application of series circuit?
- A Fuse in circuit  
B Voltmeter connection  
C Electrical lamp in homes  
D Shunt resistor in ammeter
- 11 What is the change in value of resistance of the conductor, if its cross section area is doubled?
- A No change  
B Decreases 2 times  
C Increases 2 times  
D Decreases 4 times
- 12 What is the value of resistance in an open circuit?
- A Zero  
B Low  
C High  
D Infinity
- 13 Which resistor the lowest current flows in a parallel circuit having the values of 50  $\Omega$ , 220  $\Omega$ , 450  $\Omega$  and 560  $\Omega$  connected with supply?
- A 50  $\Omega$   
B 220  $\Omega$   
C 450  $\Omega$   
D 560  $\Omega$
- 14 Which is inversely proportional to the resistance of a conductor?
- A Length  
B Resistivity  
C Temperature  
D Area of cross section

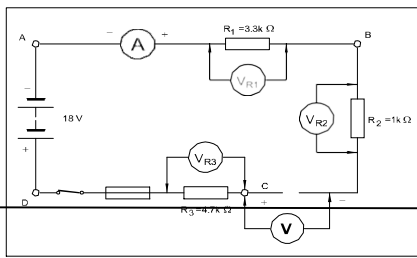15 What is the reading of the voltmeter 'V'?



- A 0 V
- B 6 V
- C 9 V
- D 18 V

16 What is the main cause for below 0.5 lagging power factor in 3 phase system?

- A Due to fluctuation of voltage
- B True power due to resistive load
- C Reactive power due to more inductive load
- D Reactive power due to more capacitive load

17 What is the current in neutral conductor in 3 phase unbalanced load in star connected system?

- A No current will flow
- B The algebraic sum of current in 3 phases
- C The algebraic sum of current in 2 phases only
- D Higher than the lowest current in any one of the phases

18 What will be the readings of two watt meters ( $W_1$  &  $W_2$ ) in 3 phase power measurement, if the power factor is zero?

- A  $W_1$  &  $W_2$  both are positive reading
- B  $W_1$  is Positive and  $W_2$  is negative reading
- C  $W_1$  is equal to  $W_2$  but with opposite signs
- D  $W_1$  is zero reading, and  $W_2$  is negative reading

19 What is the maximum value of voltage for 240 volt RMS?

- A 240V
- B 415V
- C 339.5V
- D 376.8V

20 What is the relation between the line voltage ( $V_L$ ) and phase voltage ( $V_p$ ) in star connected system?

- A  $V_L = 3\sqrt{V_p}$
- B  $V_L = 3V_p$
- C  $V_L = V_p / \sqrt{3}$
- D  $V_L = V_p / 3$


21 At what power factor in a 3 phase power measurement the reading of two wattmeters are equal and positive?

- A 0
- B 1
- C 0.5
- D 0.8

22 What is the relation between the line current ( $I_L$ ) and phase current ( $I_p$ ) in delta connected system?

- A  $I_L = I_p$
- B  $I_L = 3 I_p$
- C  $I_L = \sqrt{3} I_p$
- D  $I_L = I_p / \sqrt{3}$

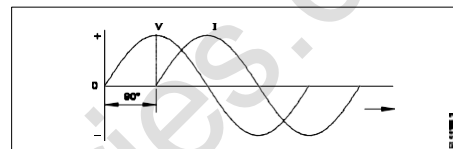23 Which AC circuit contains the phase relation between voltage (V) and current (I)?




- A Pure resistive circuit
- B Pure capacitance
- C Pure inductance
- D Pure resistance and inductance series circuit

24 In a 3 phase system, if the active power is 4 kw and the apparent power is 5 KVA, calculate the reactive power?

- A 1 KVAR
- B 2 KVAR
- C 3 KVAR
- D 4 KVAR

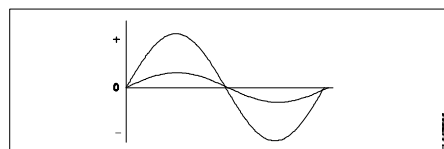25 What relationship is illustrated in between the current and voltage?



- A Current and voltage are "in phase"
- B Current and voltage are in out of phase
- C Current lags behind the voltage
- D Current leads ahead of the voltage

---

**26** Calculate the total power by two wattmeter ( $W_1$  &  $W_2$ ) method, if one of the wattmeter ( $W_2$ ) reading is taken after reversing?

- A**  $W_1 \times 2$
- B**  $W_1$  only
- C**  $W_1 - W_2$
- D**  $W_1 + W_2$


---

**27** In which 3 phase system, the artificial neutral is required to measure the phase voltage?

- A** 3 wire star connected system
  - B** 4 wire star connected system
  - C** 3 wire delta connected system
  - D** 4 wire delta connected system
-

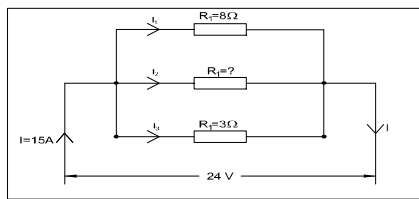
**Questions: Level 3**

- 1 Calculate the value of resistance 'R<sub>2</sub>' in the parallel circuit?




- A 2 Ω  
B 4 Ω  
C 6 Ω  
D 8 Ω

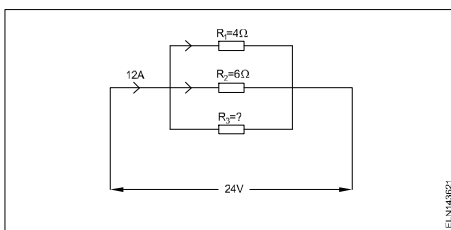- 2 Calculate the resistance value in R<sub>3</sub> resistor.



- A 4 Ohm  
B 6 Ohm  
C 8 Ohm  
D 12 Ohm

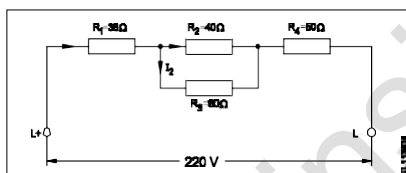- 3 Calculate the voltage drop across the resistor 'R<sub>4</sub>' in the circuit?



- A 48 V  
B 72 V  
C 80 V  
D 100 V

- 4 What happens to the voltmeter if it is connected as an ammeter?

- A Low reading  
B No deflection  
C Meter burns out  
D Overshoot deflection


- 5 What is the effect of electric current on neon lamp?

- A Heating effect  
B Magnetic effect  
C Chemical effect  
D Gas ionization effect

- 6 What is the resistance of the inductive coil takes 5A current across 240V, 50Hz supply at 0.8 power factor?

- A 48 Ω  
B 42.5 Ω  
C 38.4 Ω  
D 26.6 Ω

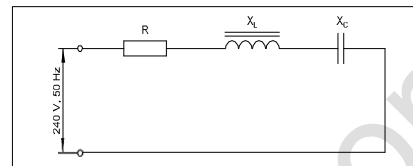- 7 Calculate the impedance of the circuit R = 5Ω, X<sub>L</sub> = 36Ω and X<sub>C</sub> = 24 Ω.?



- A 69 Ω  
B 65 Ω  
C 13 Ω  
D 12 Ω

- 8 Calculate the line current of the 3 phase 415V 50 HZ supply for the balanced load of 3000 watt at 0.8 power factor is connected in star.

- A 8.5 A  
B 5.2 A  
C 4.5 A  
D 3.4 A

- 9 Calculate the power factor of coil having resistance of 24Ω, draws the current of 5A, at 240V/ 50HZ AC supply.

- A 0.8  
B 0.6  
C 0.5  
D 0.3


- 10 Calculate the power factor of R.L.C circuit having resistance (R) = 15W, resultant reactance (X) = 20W connected across 240V /50Hz AC supply?

- A 0.5  
B 0.6  
C 0.7  
D 0.8

- 11 How the low power factor (P.F) can be improved in AC circuits?

- A By connecting resistors in series  
B By connecting capacitors in series  
C By connecting inductors in series  
D By connecting capacitors in parallel

- 
- 12 What is the P.F in 2 wattmeter method of 3 phase power measurement, if one of the wattmeters reading is zero and the other reads total power?
- A 0.5  
B Zero  
C Unity  
D Below 0.5
- 
- 13 How will you obtain positive reading in the wattmeter reads negative reading during 3-phase two wattmeter method?
- A By interchanging the connections of input terminals  
B By disconnecting the connection of current coil in meter  
C By reversing the connection of pressure coil in meter  
D By reversing the pressure coil and current coil connection in meter
- 
- 14 What is the power factor if one of the wattmeter gives negative reading in two wattmeter method of 3 phase power measurement?
- A 0.5  
B Unity  
C Between 1 to 0.5  
D Between 0.5 to zero
- 
- 15 What is the effect of the circuit, if 'ab' points are shorted?

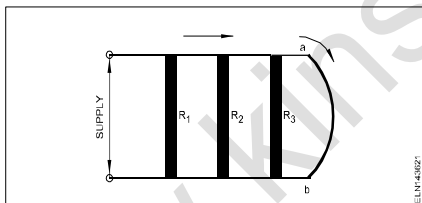

- A Circuit resistance will be zero  
B Same current will flow in all branches  
C Supply voltage will exist in each branch  
D Total circuit current is equal to each branch circuit current
-

## Module 2 : Basic Electrical - AC circuits - Key paper

### Questions: Level 1

SL.No	Key
1	D
2	D
3	B
4	C
5	C
6	A
7	A
8	C
9	B
10	C
11	C
12	D
13	B
14	D
15	D
16	B
17	D
18	A
19	B
20	B

### Questions: Level 2

SL.No	Key
1	D
2	D
3	B
4	B
5	C
6	D
7	C
8	B
9	B
10	A
11	B
12	D
13	D
14	D
15	D
16	C
17	D
18	C
19	C
20	A
21	B
22	C
23	B
24	C
25	A
26	C
27	C

### Question: Level 3

SL.No	Key
1	C
2	D
3	D
4	A
5	D
6	C
7	C
8	B
9	C
10	B
11	D
12	A
13	C
14	D
15	A